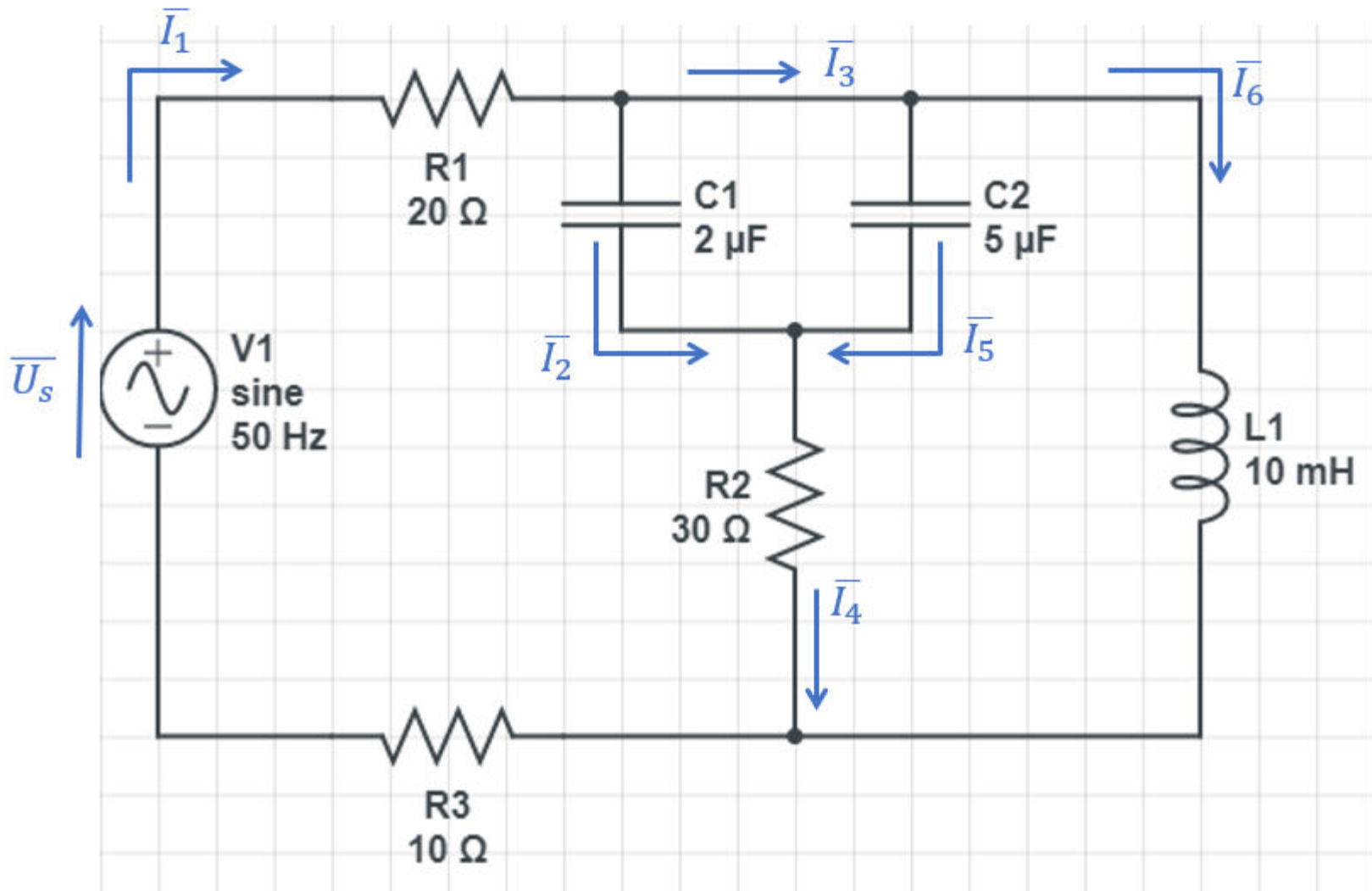


## Matrix resolution of an AC circuit via Kirchhoff, including transient

\*\*

Let's imagine the AC electrical circuit below : (already solved using phasors)



with :

- $U_s = 5 \sin\left(\omega t + \frac{\pi}{4}\right) [V]$
- $R_1 = 20 [\Omega]$
- $R_2 = 30 [\Omega]$
- $R_3 = 10 [\Omega]$
- $C_1 = 2 [\mu F]$
- $C_2 = 5 [\mu F]$
- $L = 10 [mH]$
- $f = 50 [Hz]$

You're asked to :




- Find the transfer function linking the current  $I_6(s)$  through the inductance L to the input voltage  $U_s(s)$  and check the duration of the transient. This is done on the basis of Kirchhoff's equations (previously obtained in exercise `exo_circuit_phaseurs_1`) and a matrix inversion but this time via dynamic systems and no longer complex impedances. For example : using phasors, the current in a capacitor is written  $I_c = U_c \cdot 1i \cdot \omega \cdot C$ ; using dynamical system:  $i_c = u_c \cdot s \cdot C$  (with  $s$ ; the Laplacian operator).
- Using the Bode diagram, check the steady state current obtained for the input voltage defined above.
- Represent the signal of the source voltage and that of the current (in transient and established state) in the coil as a function of time, on 2 complete periods, with 1000 points, and the same formatting as the graph below.
- Then observe the index response of this circuit (input step: `us`, output = 0)
- Draw the bode diagram of the answer (input: `us`; output: `ul`)

**Tips :** `tf('s')` `pole` `lsim` `step` `bode`

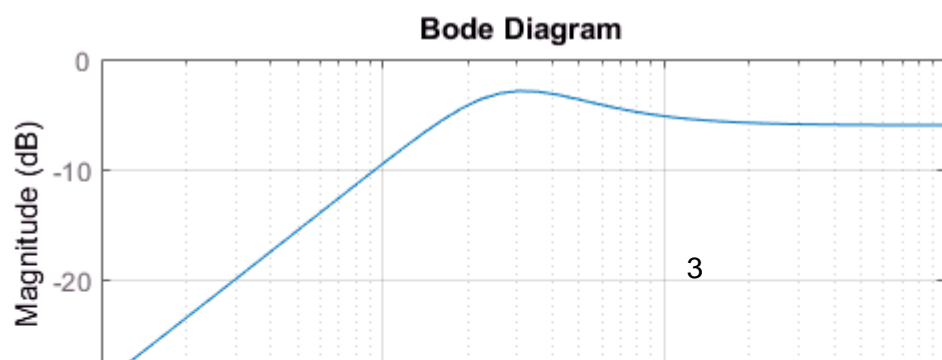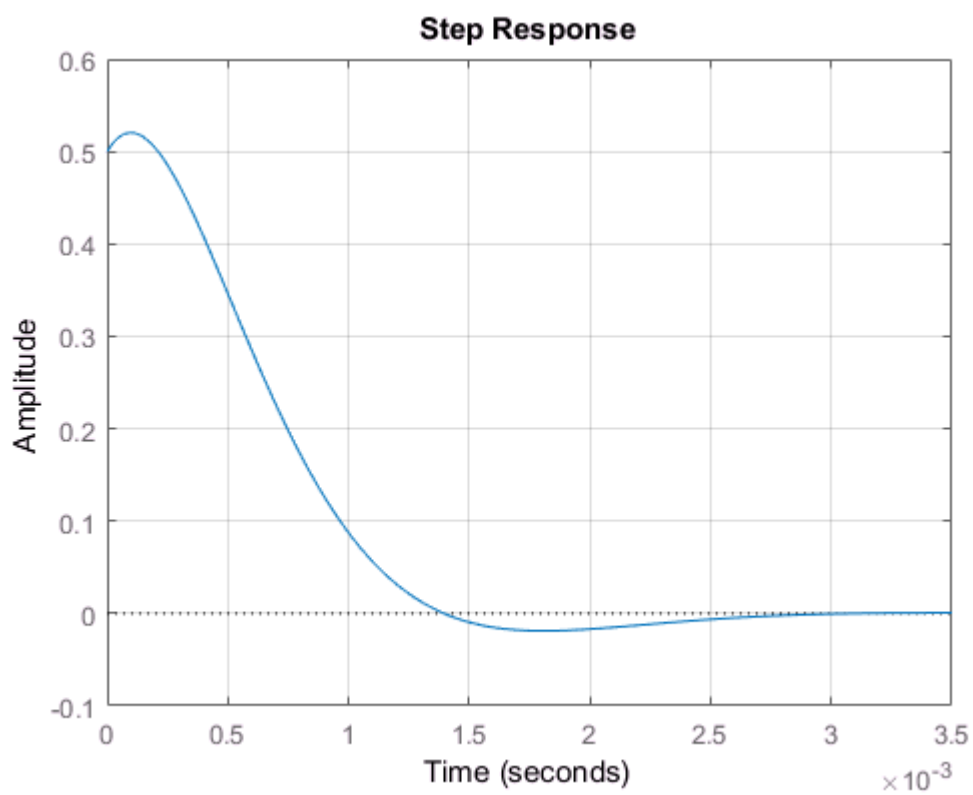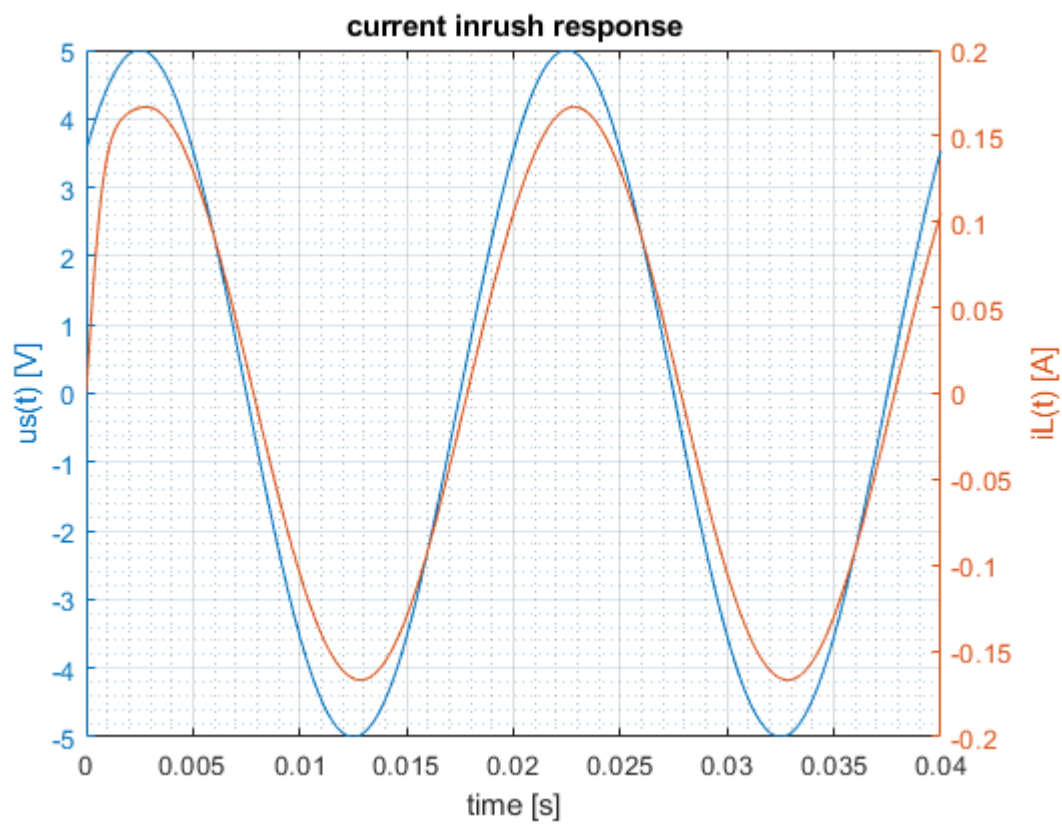**Solution:**

$$H(s) = \frac{I_6(s)}{U_s(s)} = \frac{(50s + 2.381e05)}{s^2 + 3881s + 7.143e06}$$

- **Transient duration : 2.6 ms**
- **Stead-state current : Amplitude of 0.1669 A and phase equal to 38.95°. frequency = 100 pi**



```

clear all
close all

% Encoding of all necessary parameters and creation of "impedances"
according to the variable s
R1=20;
R2=30;
R3=10;
C1=0.000002;
C2=0.000005;
L=0.010;

s=tf('s');
ZR1=R1;
ZR2=R2;
ZR3=R3;
ZC1=1/(s*C1);
ZC2=1/(s*C2);
ZL=s*L;

```

```

% First way to find the TF : thanks to matrix inversion

```

```

Z=[ZR1+ZR3  ZC1  0  ZR2  0  0;...
   0         ZC1  0  0  -ZC2  0;...
   0         0  0  ZR2  ZC2 -ZL;...
   1        -1 -1  0  0  0;...
   0         1  0 -1  1  0;...
   1         0  0 -1  0 -1];

```

```

Z1=inv(Z); % This inverted matrix contains the TF linking the circuit's
currents to the input voltage
H=minreal(Z1(6,1)) % The TF we're interested in

```

H =

$$\frac{50 s + 2.381e05}{s^2 + 3881 s + 7.143e06}$$

Continuous-time transfer function.

```

% Second way to find the TF

```

```

Z1=ZR1+ZR3; Z1=(ZR1+ZR3);
Z2=((ZC1*ZC2)/(ZC1+ZC2))+ZR2;
Zth=(Z1*Z2)/(Z1+Z2);
H=minreal((Z2/(Z1+Z2))/(Zth+ZL)) % It's the same as previously found

```

H =

$$50 s + 2.381e05$$

```
-----  
s^2 + 3881 s + 7.143e06
```

Continuous-time transfer function.

```
% Steady-state response for a 100 rad/s frequency sine sollicitation (it's %  
our input signal frequency)  
[mag,ph]=bode(H,100*pi)
```

```
mag = 0.0334  
ph = -6.0452
```

```
% Comparason to the previously solved exercise exo 1 : We found a current of  
0.1669 A and a phase of 38.95 ° when the input voltage was 5 V and 45°.  
5*mag
```

```
ans = 0.1669
```

```
45+ph
```

```
ans = 38.9548
```

```
% Plotting the time-related response for 2 periods  
f=50; w=2*pi*f; T=1/f;  
t=linspace(0,2*T,1000);  
us=5*sin(w*t+pi/4);
```


```
% Check the transient duration : Really fast!  
p1=pole(H)
```

```
p1 = 2x1 complex  
103 ×  
-1.9405 + 1.8378i  
-1.9405 - 1.8378i
```

```
Transitoire=5*-1/real(p1(1)) % in seconds
```

```
Transitoire = 0.0026
```
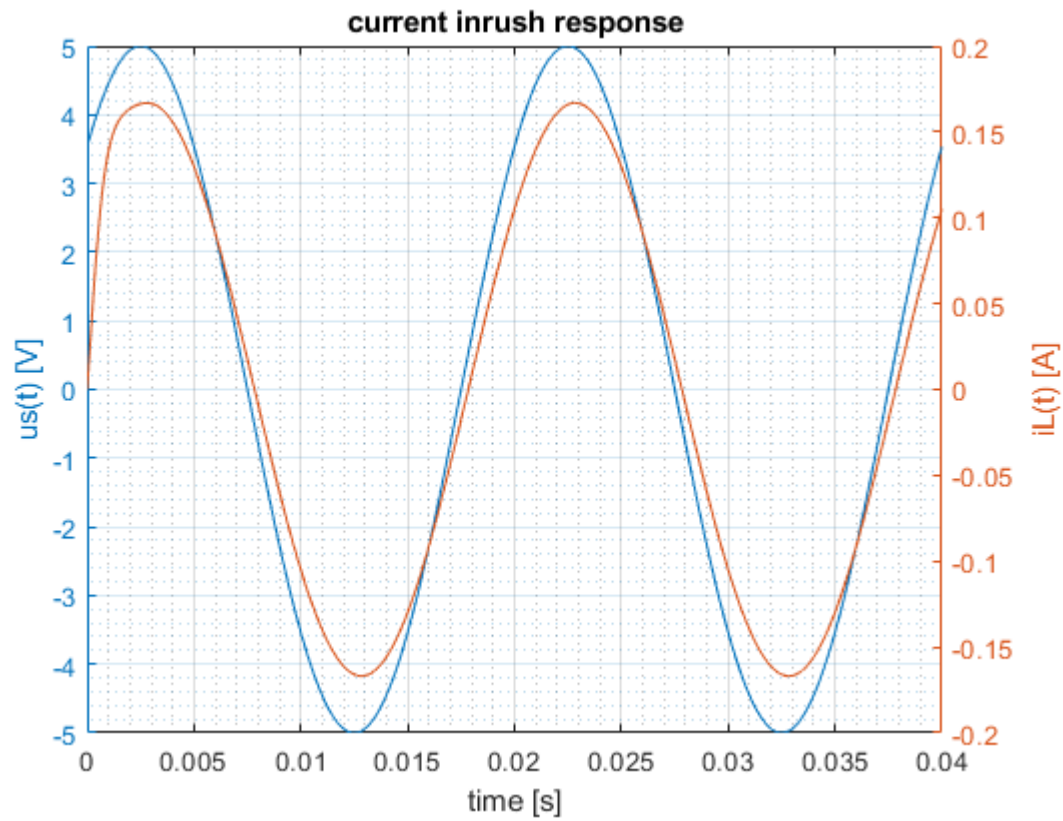
```
% PLOting the curve : one can see the transient (for about 2 ms) and the  
amplitude and phase matching what we got thanks to Bode command.  
iL=lsim(H,us,t);  
grid, grid minor  
xlabel('time [s]')  
title('current inrush response')  
yyaxis left, plot(t,us), ylabel('us(t) [V]')  
yyaxis right, plot(t,iL), ylabel('iL(t) [A]')
```



figure


```
% New FT linking Ul to Us :
G=minreal(ZL*H)
```

G =

$$\frac{0.5 s^2 + 2381 s}{s^2 + 3881 s + 7.143e06}$$

Continuous-time transfer function.

```
step(G); grid
```

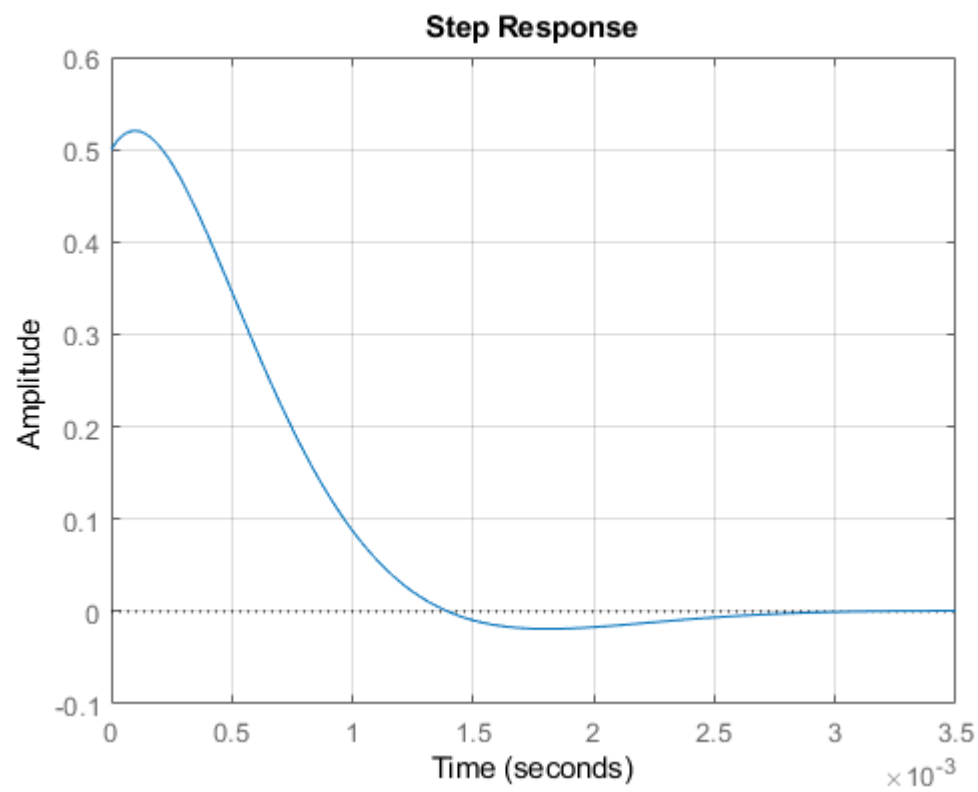

```
bode(G); grid
```

